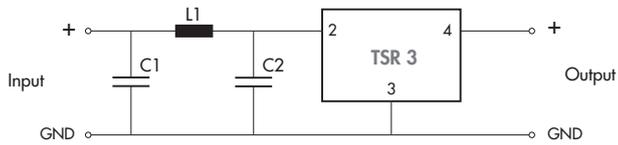
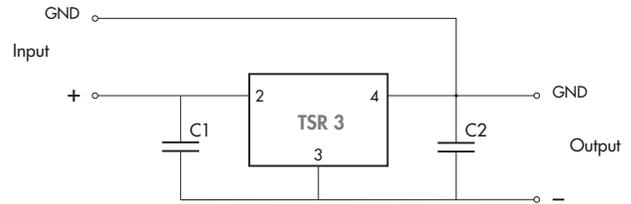


Application note**Input filter to reduce reflected ripple current****Positive output circuit**

C1 = 220 μ F, ESR < 0.1 Ohm
C2 = 150 μ F
L1 = 8.2 μ H

Negative output circuit

C1, C2 = 10 μ F (MLCC) are required and must be placed close to the converter.